

CONTENTS

Introduction	7
Chapter One. BASIC DEFINITIONS AND CONCEPTS	11
1-1. Classification of Methods of Measurement	11
1-2. General Remarks on Sensitivity	15
Chapter Two. PRIMARY AND SECONDARY STANDARDS OF ELECTRICAL UNITS	20
2-1. General	20
2-2. Standards of Resistance	22
2-3. Standards of Capacitance	25
2-4. Standards of Inductance	27
2-5. Standards of E. M. F.	29
Chapter Three. DIRECT-CURRENT AND ALTERNATING-CURRENT NULL DETECTORS	31
3-1. Types of Null Detectors	31
3-2. The Moving-coil Galvanometer	34
3-3. Valve-type A. C. Null Detectors	39
Chapter Four. AUXILIARY EQUIPMENT	53
4-1. Types of Auxiliary Equipment. Requirements	53
4-2. D. C. Power Supplies	54
4-3. Voltage Stabilizers	56
4-4. A. C. Supplies	62
4-5. Auxiliary Amplifiers	67
Chapter Five. THE D. C. BRIDGE METHOD	70
5-1. The Bridge Circuit. Definition of the Bridge Method	70
5-2. The Four-arm (Wheatstone) Bridge	71
5-3. The Kelvin Double Bridge	78
5-4. The Sensitivity of D. C. Bridges	86
5-5. Unbalanced Bridges. Comparison Sets	94
5-6. Construction of D. C. Bridges	110
Chapter Six. ALTERNATING-CURRENT BRIDGE MEASUREMENTS	114
6-1. Properties and Classification of A. C. Bridges	114
6-2. The Sensitivity of A. C. Bridges	123

6-3. Balancing and Circle Diagrams of A. C. Bridges	134
6-4. Balance Convergence of A. C. Bridges	142
6-5. Independence of Adjustments and Measurement	151
6-6. Basic Types of A. C. Bridges	156
6-7. Quasi-balanced A. C. Bridges	180
6-8. A. C. Percentage Bridges	187
Chapter Seven. THE D. C. POTENTIOMETER METHOD	193
7-1. Basic Principles and Development of the Potentiometer Method	193
7-2. Practical D. C. Potentiometers	210
7-3. The Sensitivity of D. C. Potentiometers	221
7-4. Applications of D. C. Potentiometers	227
Chapter Eight. THE ALTERNATING-CURRENT POTENTIOMETER METHOD	232
8-1. Special Features of the A. C. Potentiometer Method	232
8-2. Principles of Construction and Practical A. C. Potentiometers	236
8-3. Applications of A. C. Potentiometers	244
Chapter Nine. CONTROL OF STRAY EFFECTS	247
9-1. Principal Sources of Stray Effects	247
9-2. Control of Stray Effects in D. C. Measuring Circuits	250
9-3. Control of Stray Effects in A. C. Measuring Circuits	252
Index	263