

Contents

Chapter 1	Introduction	1
1.1	Power Electronic Circuits	1
1.2	Power Semiconductor Switches	2
1.2.1	The Diode	4
1.2.2	The Transistor	4
1.2.3	The Thyristor	4
1.3	Transformers	5
1.4	Nomenclature	8
	<i>Notes and Bibliography</i>	8
PART I FORM AND FUNCTION		9
Chapter 2	Form and Function: An Overview	11
2.1	The Functions of a Power Circuit	11
2.2	ac/dc Converters	13
2.2.1	Basic Topology and Energy Flow	13
2.2.2	Filtering	17
2.3	dc/dc Converters	20
2.3.1	Basic Topology	21
2.4	ac/ac Converters	23
2.4.1	Topologies	23
2.5	Influence of Switch Implementation	25
	<i>Problems</i>	28
Chapter 3	Introduction to Rectifier Circuits	31
3.1	Power Flow in Electrical Networks	32
3.2	Half-Wave Rectifiers	33
3.2.1	Half-Wave Rectifier with Resistive Load	33
3.2.2	Half-Wave Rectifier with Inductive Load	34
3.2.3	Half-Wave Rectifier with Freewheeling Diode	37
3.2.4	Circuit Replacement by Equivalent Source	40

3.2.5	The Periodic Steady State	40
3.3	ac Side Reactance and Current Commutation	41
3.3.1	Commutation Processes and Equivalent Circuits	41
3.3.2	Effects of Commutation	44
3.4	Measures and Effects of Distortion	45
3.4.1	Power Factor	46
3.4.2	Total Harmonic Distortion	50
	<i>Notes and Bibliography</i>	52
	<i>Problems</i>	53
Chapter 4	Bridge and Polyphase Rectifier Circuits	55
4.1	The Single-Phase Full-Wave Bridge Rectifier	56
4.1.1	Output Voltage and Power Factor of the Single-Phase Bridge	58
4.1.2	Commutation and Regulation in the Single-Phase Bridge	60
4.2	An Introduction to Polyphase Rectifier Circuits	62
4.3	Commutation in Polyphase Rectifiers	66
4.3.1	Commutation in the 3-Pulse Rectifier	66
4.3.2	Commutation in the 6-Pulse Bridge Rectifier	69
	<i>Notes and Bibliography</i>	74
	<i>Problems</i>	74
Chapter 5	Phase-Controlled Converters	79
5.1	Single-Phase Configurations	80
5.1.1	Half-Wave Controlled Rectifier with Resistive Load	80
5.1.2	Full-Wave Phase-Controlled Bridge Rectifier	83
5.1.3	Converter Power Factor	86
5.2	Phase Control with ac-Side Reactance	88
5.3	Inversion Limits	91
5.3.1	Commutation Failure	91
5.3.2	Margin Angle	94
5.4	Phase-Controlled 3-Phase Converters	96
	<i>Notes and Bibliography</i>	97
	<i>Problems</i>	97
Chapter 6	High-Frequency Switching dc/dc Converters	103
6.1	The dc/dc Converter Topology	104
6.2	The Canonical Switching Cell	109
6.3	The Direct Converter	110
6.3.1	The dc Conversion Ratio of the Direct Converter	111
6.3.2	Implementation of Switches	112

6.3.3	About the Duty Ratio	116
6.4	The Indirect Switching Converter	117
6.4.1	The dc Conversion Ratio of the Indirect Converter	117
6.4.2	Implementation of Switches	118
6.4.3	Variations on the Basic Indirect Converter Topology	119
6.5	The Choice of Capacitor and Inductor Values	122
6.5.1	A Ripple-Frequency Model for the Direct Converter	123
6.5.2	A Ripple-Frequency Model for the Indirect Converter	124
6.5.3	Minimum L and C for the Direct Converter	125
6.5.4	Minimum L and C for the Indirect Converter	128
6.5.5	Calculations for the Up/Down and Ćuk Converters	129
6.6	Semiconductor Device Stresses	130
6.7	Converter Operation with Discontinuous Conduction	132
	<i>Notes and Bibliography</i>	134
	<i>Problems</i>	134
Chapter 7	Isolated High-Frequency dc/dc Converters	139
7.1	The Single-Ended Isolated Forward Converter	140
7.1.1	Magnetizing Current and Clamping	140
7.1.2	A Transformer-Coupled Clamp	144
7.1.3	The Isolated Hybrid Bridge	146
7.1.4	Switch Stresses in the Single-Ended Isolated Converter	146
7.2	The Double-Ended Isolated Forward Converter	148
7.2.1	The Double-Ended Bridge Converter	148
7.2.2	The Double-Ended Isolated Half-Bridge Converter	152
7.3	The Flyback Converter	155
7.4	Effects of Transformer Leakage Inductance	157
7.4.1	Leakage Effects in the Single-Ended Converter	157
7.5	Converters with Multiple Outputs	161
	<i>Notes and Bibliography</i>	161
	<i>Problems</i>	162
Chapter 8	Variable-Frequency dc/ac Converters	167
8.1	The Basic Variable-Frequency Bridge Converter	168
8.1.1	Bridge Converters with Nonunity Power Factor Loads	169
8.1.2	Power Control for a Load Containing an ac Voltage Source	170
8.1.3	The Current-Source Inverter	172
8.2	Harmonic Reduction	173
8.2.1	Harmonic Elimination	174

8.2.2	Harmonic Cancellation	176
8.3	Pulse-Width Modulated dc/ac Converters	179
8.3.1	Waveshaping and Unfolding	179
8.3.2	The High-Frequency Bridge Converter	183
8.3.3	Generation of $d(t)$ for the PWM Inverter	185
8.4	Transformer-Coupled Converters	186
8.4.1	High-Frequency Transformer Isolation	186
8.5	3-Phase Converters	188
8.5.1	Evolution of the 3-Phase Inverter Circuit	188
8.5.2	Harmonics in 3-Phase Inverter-Driven Loads	191
	<i>Notes and Bibliography</i>	193
	<i>Problems</i>	193
Chapter 9	Resonant Converters	197
9.1	A Review of Second-Order System Behavior	199
9.1.1	The Time-Domain Response	199
9.1.2	The Frequency-Domain Response	200
9.2	The Voltage-Source Series Resonant Converter	202
9.2.1	The Filter	202
9.2.2	Control of the Output Waveform	202
9.2.3	Implementation of Switches	205
9.2.4	Values for L and C	205
9.2.5	Switching Losses	208
9.3	The Current-Source Parallel Resonant Converter	212
9.4	Modified Resonant Converter Topologies	217
9.4.1	Splitting the Inductor in the Voltage-Source Converter	217
9.4.2	Repositioning the Load for Lower Distortion	221
9.5	The Bridge Topology	221
9.5.1	Power Control	222
9.6	Discontinuous Mode Control	223
9.6.1	Basic Discontinuous Mode Operation	223
9.7	Resonant dc/dc Converters	226
9.7.1	Basic Topologies	227
9.7.2	Single-Ended Topologies	228
	<i>Notes and Bibliography</i>	230
	<i>Problems</i>	231
Chapter 10	ac/ac Converters	235
10.1	Energy Storage Requirements in a dc-Link Converter	237
10.2	The Naturally Commutated Cycloconverter	241
10.2.1	Principles of Operation	241
10.2.2	Cycloconverters with Polyphase Outputs	245

<i>Notes and Bibliography</i>	247
<i>Problems</i>	247

PART II DYNAMICS AND CONTROL 251

Chapter 11	Dynamics and Control: An Overview	253
11.1	Control System Configuration	254
11.2	Model Selection	259
11.2.1	The Need for Dynamic Models	259
11.3	Obtaining Dynamic Models by Circuit Averaging	261
11.3.1	Averaging a Variable	262
11.3.2	Averaging a Circuit	263
11.3.3	Averaging a Switching Function	266
11.3.4	Averaging a Switch	269
11.3.5	A Generalization: The Local ω -Component	273
11.4	Linearized Models	274
11.4.1	Linearization	274
11.4.2	Linearizing a Circuit	275
11.4.3	Linearizing the Averaged Switch	277
11.5	Feedback Control	280
11.5.1	The Classical LTI Control Configuration	280
11.5.2	Nominal Stability	284
11.5.3	Nominal Performance	287
11.5.4	Robustness	290
	<i>Notes and Bibliography</i>	293
	<i>Problems</i>	295
Chapter 12	State-Space Models	299
12.1	Features of State-Space Models	300
12.1.1	State Variables, Inputs, and Outputs	301
12.2	Continuous-Time Models	301
12.3	State-Space Models for Electrical Circuits	303
12.4	Properties of Solutions	308
12.4.1	The State Property	308
12.4.2	Numerical Solution	309
12.4.3	The Continuity Property	311
12.5	Discrete-Time or Sampled-Data Models	313
12.6	Notation	315
12.7	Generalized State-Space Models	319
12.8	Models for Controllers and Interconnected Systems	323
	<i>Notes and Bibliography</i>	325
	<i>Problems</i>	326

Chapter 13	Linear and Piecewise Linear Models	329
13.1	Linearization	329
13.2	Linearizing Continuous-Time Models	330
13.3	Analysis of Continuous-Time LTI Models	333
13.3.1	Transform-Domain Solution	334
13.3.2	Time-Domain Solution	338
13.4	Piecewise LTI Models	344
13.5	Linearizing Discrete-Time Models	347
13.6	Analysis of Discrete-Time LTI Models	352
13.6.1	Time-Domain Solution	352
13.6.2	Transform-Domain Solution	353
13.6.3	Transfer Functions and Frequency Response	357
	<i>Notes and Bibliography</i>	360
	<i>Problems</i>	362

Chapter 14	Feedback Control Design	365
14.1	Classical Control Design	366
14.1.1	The Nyquist Stability Criterion	366
14.1.2	A Design Approach	368
14.1.3	Using Bode Plots	370
14.1.4	Designing the Bode Plots of the Loop Gain	373
14.2	Multiloop Control	379
14.2.1	Current-Mode Control	380
14.3	State Feedback	389
14.3.1	Pole Placement by LTI State Feedback	390
14.3.2	Nonlinear State Feedback	393
14.4	Digital Control	395
	<i>Notes and Bibliography</i>	399
	<i>Problems</i>	400

PART III COMPONENTS AND DEVICES 403

Chapter 15	Components: An Overview	405
15.1	Practical Semiconductor Switches	406
15.2	Practical Energy Storage Elements	407
15.3	Power Semiconductor Devices	407
15.3.1	The Power Diode	408
15.3.2	The Power Transistor	410
15.3.3	The Thyristor	420
15.4	Capacitors	425
15.4.1	Film Capacitors	426
15.4.2	Electrolytic Capacitors	426

15.4.3	Multilayer Ceramic Capacitors	427
15.5	Inductors and Transformers	428
15.5.1	Magnetic Materials	429
15.5.2	Magnetic Core Geometries	429
15.5.3	Losses in Magnetic Components	430
	<i>Problems</i>	431

Chapter 16	Review of Semiconductor Devices	435
16.1	Elementary Physics of Semiconductors	435
16.1.1	Charge Carriers in a Semiconductor	435
16.1.2	Charge Transport in Semiconductors	439
16.1.3	The pn Junction in Thermal Equilibrium	442
16.2	Simple Diode Analysis	446
16.2.1	Dependence of the SCL Width on v_A	446
16.2.2	Incremental Capacitance of the SCL	447
16.2.3	Carrier Concentrations at the Edge of the SCL	447
16.2.4	Determination of Diode Current	448
16.3	The Bipolar Transistor	452
16.3.1	Physical Model and Terminal Currents	452
16.3.2	Device Parameters	454
16.3.3	The Ebers–Moll Model of an npn Transistor	457
16.3.4	Saturation	458
16.4	The MOSFET	458
16.4.1	MOSFET Characteristics	460
16.4.2	The Dependence of V_T on Substrate Potential	462
	<i>Notes and Bibliography</i>	462
	<i>Problems</i>	463

Chapter 17	Power Diodes	469
17.1	The Bipolar Diode under Reverse Bias	469
17.1.1	Leakage Current	469
17.1.2	Avalanche Breakdown	472
17.2	The pin Diode	475
17.2.1	Forward Bias	477
17.2.2	Minority Carrier Diffusion Currents in the End Regions	481
17.2.3	Reduction of L_a at High Current Levels	483
17.2.4	Temperature Dependence of J	483
17.3	Switching Transitions in a pin Diode	484
17.3.1	Forward Recovery	484
17.3.2	Reverse Recovery	486
17.4	The Schottky Barrier Diode	488
17.4.1	The Schottky Barrier	488

17.4.2	Forward Bias	490
17.4.3	Reverse Bias	494
17.4.4	Switch Transitions in a Schottky Diode	495
17.4.5	Selection of Barrier Metal	496
	<i>Notes and Bibliography</i>	496
	<i>Problems</i>	497

Chapter 18 Power Transistors 499

18.1	Structure of the Power BJT	499
18.2	Operating Regions of the Power BJT	500
18.2.1	The Cutoff Region	501
18.2.2	Forward-Active Region	504
18.2.3	Quasi-Saturation Region	505
18.3	Quasi-Saturation Voltage	510
18.4	Hard-Saturation Region	511
18.5	Common Emitter-Current Gain	512
18.5.1	About the Current-Gain Parameter	513
18.6	Temperature Dependence of β	516
18.7	Switching Transitions	516
18.8	Emitter-Current Focusing during Turn-Off	521
18.9	Second Breakdown	522
18.10	Thermal Instability	526
18.11	Structure of the Power MOSFET	526
18.12	On-State Resistance of the MOSFET	528
18.12.1	Resistance of the Extended Drain Region	529
18.12.2	Resistance of the Neck Region	531
18.12.3	Resistance of the Accumulation Layer	532
18.12.4	Resistance of the Channel	532
18.12.5	Temperature Dependence of $R_{DS(on)}$	533
18.13	Dynamic Performance of the Power MOSFET	533
18.14	The Body Diode of a Vertical Power MOSFET	536
18.15	The Parasitic Bipolar Transistor	536
18.16	The Insulated Gate Bipolar Transistor	536
	<i>Notes and Bibliography</i>	538
	<i>Problems</i>	539

Chapter 19 Thyristors 541

19.1	The SCR Structure	541
19.2	Overview of SCR Operation	542
19.2.1	The Off State	543
19.2.2	The Regenerative Turn-On Process	544
19.2.3	The On State	545
19.3	The Off State	545

19.3.1	The Reverse Blocking Voltage	545
19.3.2	The Forward Blocking Voltage	548
19.3.3	Temperature Dependence of the SCR Voltage Limits	550
19.4	The Turn-On Process	551
19.4.1	The Gate-Cathode Short	552
19.4.2	Current Spreading During Turn On	553
19.5	The Turn-Off Process	554
19.5.1	Turn-Off Time and Rate Effects	555
19.6	The Gate Turn-Off Thyristor (GTO)	557
19.7	Other Thyristor Structures	559
19.7.1	The Reverse Conducting Thyristor	560
19.7.2	The TRIAC	560
19.7.3	The MOS Controlled Thyristor	561
	<i>Notes and Bibliography</i>	563
	<i>Problems</i>	563

Chapter 20 Magnetic Components 565

20.1	The Inductor	566
20.1.1	Calculating Inductance	567
20.1.2	Electric Circuit Analogs	569
20.1.3	Second-Order Effects in Determining Inductance	574
20.1.4	Energy Storage	575
20.2	Saturation, Hysteresis, and Residual Flux	577
20.2.1	Saturation	578
20.2.2	Residual Flux Density	578
20.3	Losses in Magnetic Components	581
20.3.1	Copper Loss	581
20.3.2	Core Loss	583
20.3.3	A Simple Loss Model	584
20.3.4	Why Use a Core?	586
20.4	Transformers	587
20.4.1	The Ideal Transformer	588
20.4.2	Magnetizing Inductance	589
20.4.3	Leakage Inductance	591
20.4.4	Equations for a Nonideal Transformer	594
20.4.5	Energy Storage Transformers	596
20.4.6	Current and Potential Transformers	597
20.4.7	Transformers with More Than Two Windings	599
20.5	Magnetic Material Properties	600
	<i>Notes and Bibliography</i>	601
	<i>Problems</i>	602

PART IV ANCILLARY ISSUES 607

Chapter 21 Ancillary Issues: An Overview 609

- 21.1 Gate and Base Drives 609
 - 21.1.1 BJT Base Drives 609
 - 21.1.2 MOSFET Gate Drives 610
 - 21.1.3 Thyristor Gate Drives 611
 - 21.2 Thyristor Commutation Circuits 612
 - 21.2.1 A Simple Commutation Circuit 612
 - 21.2.2 Limitations of Forced Commutation 613
 - 21.2.3 Types of Commutation Circuits 614
 - 21.3 Snubbing 614
 - 21.4 Thermal Considerations 616
 - 21.4.1 Thermal Models 616
 - 21.4.2 Heatsinking 617
- Problems* 618

Chapter 22 Gate and Base Drives 621

- 22.1 Bipolar Transistor Base Drives 622
 - 22.1.1 The Turn-On Problem 622
 - 22.1.2 The Turn-Off Problem 624
 - 22.1.3 The Darlington Connection 625
 - 22.1.4 Practical Implementation 626
 - 22.1.5 Transformer-Coupled Drives 629
 - 22.1.6 Proportional Base Drives 632
 - 22.1.7 Emitter Switching 634
 - 22.2 MOSFET Gate Drives 636
 - 22.2.1 Gate-Drive Requirements 636
 - 22.2.2 Parallel Operation of MOSFETs 638
 - 22.3 Thyristor Gate Drives 639
 - 22.3.1 Gate-Drive Requirements 639
 - 22.3.2 Optically Isolated Drives 641
 - 22.3.3 Transformer-Isolated Drives 643
 - 22.3.4 GTO Gate Drives 646
- Notes and Bibliography* 648
Problems 649

Chapter 23 Thyristor Commutation Circuits 653

- 23.1 Voltage Commutation 653
- 23.2 Current Commutation 658
- 23.3 Energy Recovery 662
 - 23.3.1 Complementary Commutation 664
 - 23.3.2 An Energy Recovery Network 666

Notes and Bibliography 667*Problems* 667

Chapter 24 Snubber Circuits and Clamps 671

- 24.1 The Turn-Off Snubber 672
 - 24.1.1 Turn-Off Dissipation and the SOA 672
 - 24.1.2 A Basic Turn-Off Snubber 674
 - 24.1.3 A More Practical Snubber 676
 - 24.2 The Turn-On Snubber 676
 - 24.2.1 Turn-On Dissipation and the SOA 676
 - 24.2.2 A Basic Turn-On Snubber 677
 - 24.2.3 A Practical Turn-On Snubber 678
 - 24.3 A Combined Turn-On/Turn-Off Snubber 679
 - 24.4 Alternative Placements of the Snubber Circuits 682
 - 24.5 Dissipation in Snubber Circuits 683
 - 24.5.1 Separate Turn-On and Turn-Off Snubbers 683
 - 24.5.2 The Combined Snubber 684
 - 24.5.3 Increased Circuit Dissipation Caused by Snubbers 684
 - 24.6 Energy Recovery Snubber Circuits 686
 - 24.7 Voltage Clamps 688
- Notes and Bibliography* 689
Problems 690

Chapter 25 Thermal Modeling and Heat Sinking 693

- 25.1 Static Thermal Models 694
 - 25.1.1 Analog Relations for the dc Case 694
 - 25.1.2 Thermal Resistance 696
 - 25.2 Thermal Interfaces 698
 - 25.2.1 Practical Interfaces 701
 - 25.2.2 The Convective Interface 701
 - 25.3 Transient Thermal Models 703
 - 25.3.1 A Lumped Model and Transient Thermal Impedance 704
- Notes and Bibliography* 709
Problems 710

List of Symbols 713

Index 715