

TABLE OF CONTENTS

Chapter 1 - Bioelectricity	1
Electrical Potentials	1
Electrical Currents.....	1
Resistors and Conductors.....	3
Ohm's Law	5
The Voltage Divider.....	6
Perfect and Real Electrical Instruments.....	7
Ions in Solutions and Electrodes	8
Capacitors and Their Electrical Fields.....	10
Currents Through Capacitors.....	11
Current Clamp and Voltage Clamp.....	13
Glass Microelectrodes and Tight Seals.....	14
Further Reading.....	16
Chapter 2 - The Laboratory Setup	17
The <i>In Vitro</i> Extracellular Recording Setup	17
The Single-Channel Patch Clamping Setup.....	18
Vibration Isolation Methods	18
Electrical Isolation Methods	19
Radiative Electrical Pickup	19
Magnetically-Induced Pickup	20
Ground-Loop Noise.....	20
Equipment Placement	20
List of Equipment.....	22
Further Reading.....	24
Chapter 3 - Instrumentation for Measuring Bioelectric Signals from Cells	25
Extracellular Recording	25
Single-Cell Recording	26
Multiple-Cell Recording	27
Intracellular Recording — Current Clamp	27
Voltage Follower.....	27
Bridge Balance	29
Junction Potentials	30
Track.....	30
Current Monitor.....	31
Headstage Current Gain	33
Capacitance Compensation	33
Transient Balance	37
Leakage Current	37
Headstages for Ion-Sensitive Microelectrodes	37



Bath Error Potentials	38
Cell Penetration: Mechanical Vibration, Buzz and Clear	42
Command Generation	43
Intracellular Recording — Voltage Clamp	43
The Ideal Voltage Clamp	44
Real Voltage Clamps.....	44
Large Cells — Two-Electrode Voltage Clamp	45
Small Cells — Discontinuous Single-Electrode Voltage Clamp.....	48
Discontinuous Current Clamp (DCC).....	54
Continuous Single-Electrode Voltage Clamp	54
Series Resistance Compensation.....	56
Pipette-Capacitance Compensation.....	60
Whole-Cell Capacitance Compensation	62
Rupturing the Patch.....	64
Which One Should You Use: dSEVC or cSEVC?.....	65
Space Clamp Considerations.....	65
Single-Channel Patch Clamp	66
The Importance of a Good Seal.....	67
Resistor Feedback Technology	67
Capacitor Feedback Technology	70
Special Considerations for Bilayer Experiments	73
How Fast is "Fast"?	74
Measurement of Changes in Membrane Capacitance.....	74
Seal and Pipette Resistance Measurement	75
Micropipette Holders	75
Current Conventions and Voltage Conventions.....	76
Definitions.....	76
Whole-Cell Voltage and Current Clamp.....	77
Patch Clamp	78
Summary	79
References	80
Chapter 4 - Microelectrodes and Micropipettes	81
Electrodes, Microelectrodes, Pipettes, Micropipettes and Pipette Solutions	81
Fabrication of Patch Pipettes	83
Pipette Properties for Single-Channel vs. Whole-Cell Recording.....	84
Types of Glasses and Their Properties.....	85
Thermal Properties of Glasses	86
Noise Properties of Glasses.....	87
Leachable Components	89
Further Reading.....	89



Chapter 5 - Advanced Methods In Electrophysiology	91
Recording from <i>Xenopus</i> Oocytes	91
What is a <i>Xenopus</i> Oocyte?.....	92
Two-Electrode Voltage Clamping of Oocytes.....	93
Patch Clamping <i>Xenopus</i> Oocytes	95
Further Reading.....	95
Patch-Clamp Recording in Brain Slices	96
The Cleaning Technique	96
The Blind Technique.....	99
Advantages and Disadvantages of the Two Methods of Patch Clamping Brain Slices	101
Further Reading.....	102
Macropatch and Loose-Patch Recording.....	103
Gigaseal-Macropatch Voltage Clamp.....	103
Loose-Patch Voltage Clamp.....	104
References.....	109
The Giant Excised Membrane Patch Method	111
Pre-Treatment of Muscle Cells	111
Pipette Fabrication	112
Seal Formation	113
Further Reading.....	113
Recording from Perforated Patches and Perforated Vesicles.....	114
Properties of Amphotericin B and Nystatin.....	114
Stock Solutions and Pipette Filling.....	114
Properties of Antibiotic Partitioning.....	115
The Advantages of the Perforated-Patch Technique.....	115
The Limitations of the Perforated-Patch Technique.....	116
Suggested Ways to Minimize the Access Resistance	117
Other Uses for Perforated Patches	118
Further Reading.....	121
Enhanced Planar Bilayer Techniques for Single-Channel Recording.....	122
I. Solving the Problems of High Resolution and Voltage Steps.....	122
Minimizing the Background Current Noise.....	122
Maximizing the Bandwidth.....	125
Resolving Voltage Steps Across Bilayers.....	125
II. Assembling a Bilayer Setup for High-Resolution Recordings	127
Choosing an Amplifier.....	127
Choosing a Recording Configuration.....	128
Making Small Apertures	128
Viewing with a Microscope	130
Testing the System	130
Making the Recordings	131
Further Reading.....	132